# 16-bit custom RISC ISA pipelined processor with floating point Coprocessor

### NCHU VLSI-CAD Final Project

Shun-Linag Yeh, NCHU Lab612

Instructor: Prof. Hun-Chun Lin

December 2022

Github: Click for Github Link

### **INDEX**

- 1. Introduction
- 2. Instruction Set Architecture
- 3. High level design
- 4. Software
- 5. MicroArchitecture
- 6. Results
- 7. FutureWorks
- 8. Acknowledgements
- 9. References

### I. Introduction

In this project, I implemented a 5-stages custom RISC pipelined processor. To ensure performance and prevent wasted cycle due to stall, hazard units with stall control to resolve lw-r hazard, r-r hazard and control hazard is implemented.

This processor supports a small subset of Custom RISC-ISA, it supports ADD,SUBTRACTION,LW,SW and basic control flow instruction JUMP and JMPZ. Additional instruction like ADDF and MULTF are also implemented to support the basic floating point arithmetic.

The whole processor is built upon the Von-Neuman architecture. For simplicity, ideal memory is considered in this project. As a result, the instructions and data will be first loaded into the D-MEM and I-MEM in testbench then get fed into the processor.

The processor is divided into 5-stage, Instruction Decode(ID) stage Instruction Fetch(IF) stage Execution(EX) stage Memory access(MEM) stage Write Back(WB) stage.

# II. Custom Instruction Set Architecture(ISA)

The custom ISA I used is different from the original MIPS ISA, the original reference is from one of my lab senior past course where he implemented a multicycle processor under this ISA. This ISA has 2 types of instruction, R-type which performs numerical operation and floating point operations and I-type which performs immediate operation and Load-store memory.

R-type	OP[15:12]	rs[11:8]	rt[7:4]	rd[3:0]	JMPZ	
add	`0010				Jump to PC	C+imm8  if  R[rs] == 0
sub	`0100					
addf	`1000					
multf	`1001					
					MOV	
I-type	OP[15:12]	rs[11:8]	imm	8[7:0]	R[rs]<-Sign	n Extend(imm8)
mov	`0011					
jmpz	`0101				SW	
jump	`0110				R[rs] -> Da	ntaMemory[imm8]
stop	`0111					
SW	`0001				LW	
lw	`0000				R[rs] <- D1	M[imm8]
					Jump	
					Jump to &	mm8

### R-type

In this ISA, R-type has the same format as MIPS ISA.

	4-bit Opcode	Source Register1	Source Register2	Destination Register
R-type	OP[15:12]	rs[11:8]	rt[7:4]	rd[3:0]

### I-type


I-type is different where source register is removed and the destination register \$rt get replaced by \$rs.

	4-bit Opcode	Destination Register	8-bit Immediate field
I-type	OP[15:12]	rs[11:8]	imm8[7:0]

# III. High Level Design


Partition the whole system into testbench, main processor and floating point coprocessor

### System Diagram

 
 
# 16-bit IEEE Floating-point format

IEEE-754 half precision floating point format is used for the implementation of my Coprocessor.



## IV. Software

I provided 6 test cases written in assembly code for my processor, each tests resolves some issues for my processor. To ensure that my processor is working as expected. Below is one of my test case.

#### Test5

```
int a = 3;
int b = 4;
int c = 0;
if(a == 3)
    c = a + b;
else
    c = 10;

D[0] = c;
```

#### Assembly

```
0:
              mov \$0,3 # a = 3
              mov $1,4 # b = 4
1:
              mov $2,0 # c = 0
2:
              mov $6,3 # $t1 = 3
3:
              sub \$8,\$0,\$6 # if((a-3 == 0))
4:
5:
              jmpz $8,if
6:
              mov $2,10
7:
                   endif
              add $2,$0,$1 # c = a + b
8:if:
9:endif:
              sw \$2,0 # D[0] = c = 7;
nop
nop
nop
nop
nop
nop
nop
stop
```


#### Machine Code

```
0: 0011_0000_0000_0011
1: 0011_0001_0000_0100
2: 0011_0010_0000_0000
3: 0011_0110_0000_0011
4: 0100_0000_0110_1000
5: 0101_1000_0000_1000
6: 0011_0010_0000_1010
7: 0110_1111_0000_1001
8: 0010_0000_0001_0010
9: 0001_0010_0000_0000
10:1111_0000_0000_0000
   1111_0000_0000_0000
   1111_0000_0000_0000
   1111_0000_0000_0000
   1111_0000_0000_0000
   1111_0000_0000_0000
   1111_0000_0000_0000
   0111_0000_0000_0000
```

# V. MicroArchitecture
 
### Processor block diagram

The processor is divided into 3 parts. Main pipelined datapath for the data flow and 2 controls units. One for Hazard handling and one as Main CTR to govern the flow control in the datapath.



# Control path


#### Main Control

The decoded control vector is provided for the OP code given. The control vector would govern the data flow within the processor.

	OP	RegWrite	ALUOP	Branch	MemRead	RegDst	MemWrite	Jump	MemtoReg	MOV	floating	stop
add	`0010	1	0	0	0		0		0	0	0	0
SW	`0001	0	X	0	0	X	1	0	X	X	0	0
lw	`0000	1	X	0	1	1	0	0	1	X	0	0
sub	`0100	1	1	0	0	0	0	0	0	0	0	0
mov	`0011	1	X	0	0	1	0	0	0	1	0	0
jmpz	`0101	0	0	1	0	0	0	0	0	0	0	0
jump	`0110	0	0	0	0	0	0	1	0	0	0	0
stop	`0111	0	0	0	0	0	0	0	0	0	0	1
addf	`1000	1	X	0	0	X	0	0	X	X	1	0
multf	`1001	1	X	0	0	X	0	0	X	X	1	0
NOP	`1111	0	0	0	0	0	0	0	0	0	0	0
	16	6-bit Instruct	ion									
Instruction	onType											
I-type	OP[15:12]	rs[11:8]	imm8	[7:0]								
R-type	X	rs[11:8]	rt[7:4]	rd[3:0]								
 
## **Hazard Units**

Hazard units comprised of 3 parts. Forwarding units which resolves the R-R and sw-r hazards. Stall detection units which resolves the R-LW hazards. Control hazard Handler which handles control stall and flush



# Forwarding Condition

To solve Data hazard including R-R,sw-lw

ALU\_src1:

```
// In this ISA, lw does not need forwarding. also $0 can store value other
than 0. Different from MIPS.
  if((rsE == WriteRegM) and (RegWriteM == 1) and (MemReadE != 1))
     ALU_src1 = 01
  else if ((rsE == WriteRegW) and (RegWriteW ==1) and (MemReadE != 1))
     ALU_src1 = 10
  else
     ALU_src1 = 00
```

ALU\_src2:

```
if((rtE == WriteRegM) and (RegWriteM == 1) and (MemReadE != 1))
    ALU_src2 = 01
else if ((rtE == WriteRegW) and (RegWriteW == 1) and (MemReadE != 1))
    ALU_src2 = 10
else
    ALU_src2 = 00
```

MemSrc:

To solve sw-lw data hazard

```
if((rsM == WriteRegW) and (MemReadW == 1) and (MemWriteM == 1))
    MemSrc = 1
else
    MemSrc = 0
```

### **Stall Condition**

#### To solve lw-r data hazard and stop signal

```
if(stop)
    stall Every Pipeline and PC
    else if( ((rsD==rsE) or (rtD == rsE)) and (MemReadE == 1) and (ID stage is R-type))
    stall PC and flush ID/EX
    else
        do nothing
```


#### Control Hazard Control

#### To solve j and branch hazard

```
if (PCSrc == 1 || jump == 1)
    flush EX/MEM and flush IF/ID and stallPC for 3 cycles
else
    do nothing
```
 
# Datapath


The detailed structure of my pipelined datapath.




# VI. Results

### Simulation Results waveform of Test5



 


 

# Synthesis Report

Specs	Description	Value		
Speed	Max Frequency	200Mhz		
Area	Size of chip	23517.47		
Power	power rating	1.8639mW		

# Hardware APR

 

### VII. Future Works

- 1. Branch Predictor can be added to further improve performance.
- 2. Practical memory with full memory hiearchy can be added to replace the I-MEM and D-MEM including caches.
- 3. Can add Exception handling mechanism.
- 4. Virtual address translation system and TLB can be implemented.

### VIII. Acknowledgements

I would like to ackowledge Professor Lin for his precious insight throughout the whole CAD course. Also I want to thanks the support from my Lab seniors Hun-Rui Chan and Mo-xuan Xiongs' mentorship and guidance throughout the research, design and implementation of this project. Without them, there would be no final implementation of this project.

### IX. References

- [1] Yamin Li and Wanming Chu, "Aizup-a pipelined processor design and implementation on XILINX FPGA chip," 1996 Proceedings IEEE Symposium on FPGAs for Custom Computing Machines, 1996, pp. 98-106, doi: 10.1109/FPGA.1996.564755.
- [2] N. Manjikian and J. Roth, "Performance enhancement and high-level specification of a pipelined processor in programmable logic," 2007 IEEE Northeast Workshop on Circuits and Systems, 2007, pp. 1340-1343, doi: 10.1109/NEWCAS.2007.4488017.
- [3] K. D. Rao, P. V. Muralikrishna and C. Gangadhar, "FPGA Implementation of 32 Bit Complex Floating Point Multiplier Using Vedic Real Multipliers with Minimum Path Delay," 2018 5th IEEE Uttar Pradesh Section International Conference on Electrical, Electronics and Computer Engineering (UPCON), 2018, pp. 1-6, doi: 10.1109/UPCON.2018.8597031.
- [4] David Money Harris, Sarah L. Harris, "Digital Design and Computer Architecture 2nd edition", Morgan Kaufmann, 2012.
- [5] Onur Mutlu, "Digital Design & Computer Architecture (ETH Zürich, Spring 2020)"